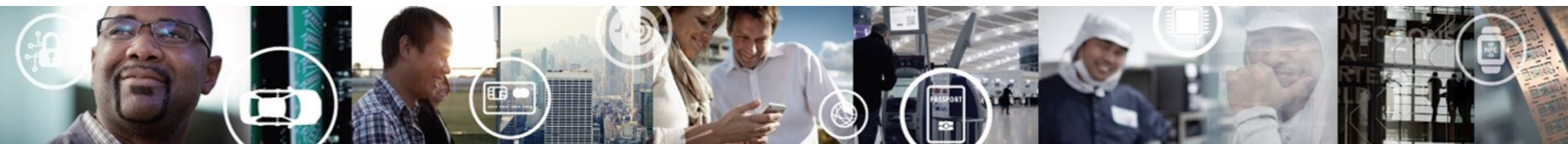


MRF300A/BN

1.8 – 150 MHz Two Tone CW

MAR 18, 2019





SECURE CONNECTIONS
FOR A SMARTER WORLD

Specifications

- Drain voltage: $V_{DD} = 50 \text{ V}$
- Quiescent current: $I_{DQ} = 500 \text{ mA}$
- Test signal: Two tone CW, 10 KHz tone spacing
- Test frequencies: 1.8, 3.5, 7, 10, 20, 30, 50, 100, 150 MHz
- Pout = 200 W Average (400W PEP)
 - Gain > 17 dB
 - IRL < -8 dB
 - Eff > 34%
 - IM3_L/U: < -24 dBc (below 1 tone, ie -30 dBc below PEP)

Assembly

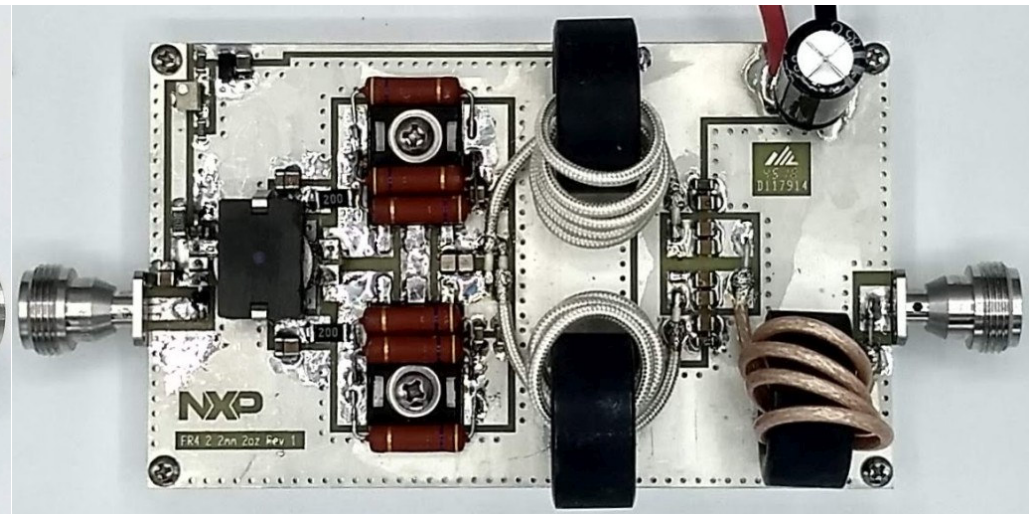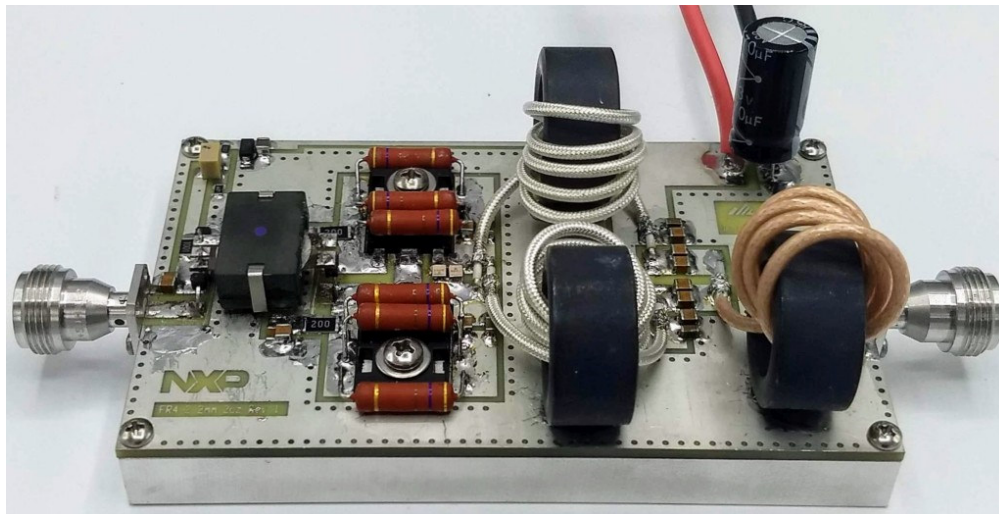

Assembly – input transformer (T1)



Step 1: Put first O-ring on EQ core




Step 2: Put planar balun (M204548) and second O-ring on EQ core




Step 3: Put plate on top of EQ core



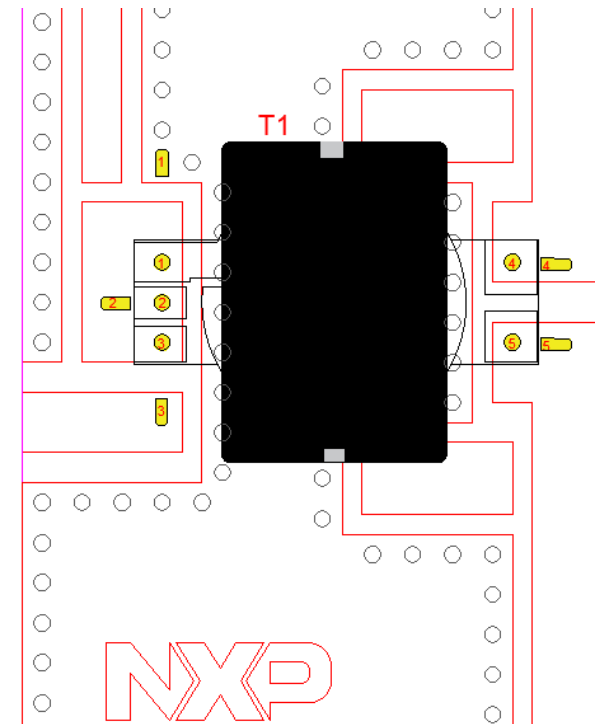Step 3: Firmly press the whole assembly together and put the clip on until you hear “click” on both edges.



Assembly

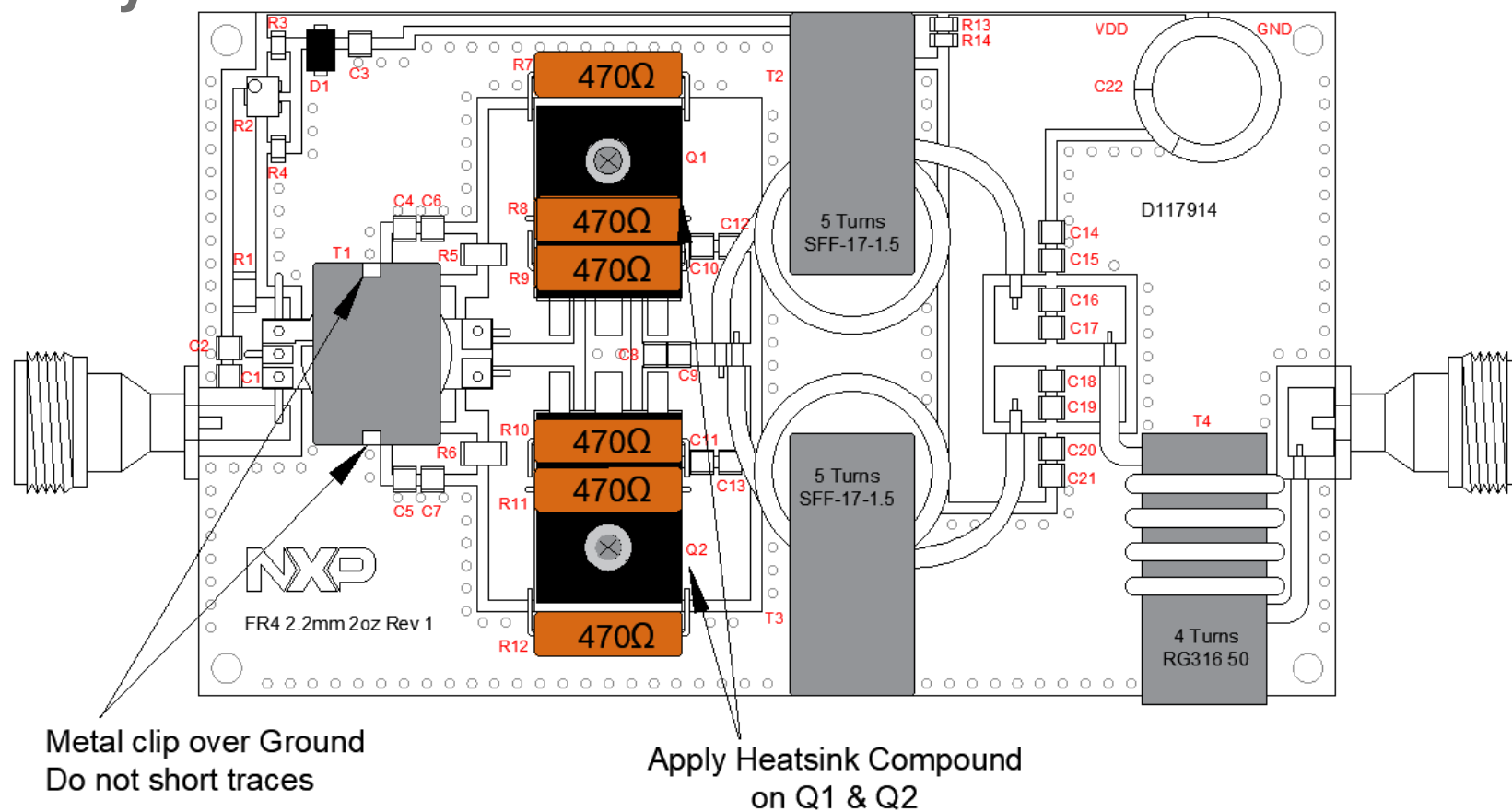

Bill of Material

Designator	Description	Part Number	Manufacturer
C1,C6,C7,C10,C11,C15,C16 C17,C18,C19,C20	10,000 pF chip capacitors	200B103KT50XT	ATC
C2,C4,C5	1 μ F 50 V chip capacitors	GRM31MR71H105KA88L	Murata
C3	10 μ F 50 V chip capacitor	GRM32ER61H106KA12L	Murata
C8,C9	30 pF chip capacitors	100B300JT500XT	ATC
C12,C13,C14,C21	1 μ F 100 V chip capacitors	GRM31CR72A105KA01L	Murata
C22	470 uF 63V Electrolytic capacitor	MCGPR63V477M13X26	Multicomp
D1	8.2V Zener Diode	SMAJ4738A	Micro Commercial Co
Q1	LDMOS transistor	MRF300AN	NXP
Q2	LDMOS transistor	MRF300BN	NXP
R1	1K Ω 2010 Chip Resistor	CRCW20101K00FKEF	Vishay
R2	SMT Trim Pot 5K, (12 turn)	3224W-1-502E	Bourns
R3	10 K Ω 1206 Chip Resistor	CRCW120610K0JNEA	Vishay
R4	5.6 K Ω 1206 Chip Resistor	CRCW12065K60FKEA	Vishay
R5,R6	20 Ω 2512 Chip Resistors	CRCW251220R0JNEG	Vishay
R7,R8,R9,R10,R11,R12	470 Ω , 5% 3W Metal Film Resistors	PR03000204700JAC00	Vishay
R13,R14	20 K Ω 1206 Chip Resistor	CRCW120620K0FKEA	Vishay
T1 Core 1	79 material EQ core	9579200602	Fair-Rite
T1 Core 2	79 material plate	9379054002	Fair-Rite
T1 PCB	1 to 4 planar balun	M204548	MTL
T1 O-ring, X2	EPDM rubber, ID 0.364", OD 0.504"	1289N112	McMaster-Carr
T1 clip	U shaped clip	1779-1293-ND	Digi-Key
T2,T3,T4 Core	61 material Ferrite Toroid	FT-114A-61	Amidon Inc
T2,T3 Cable	0.059" Dia, 17 Ω , Semi-Flex Coax 15" long, 5 turns	SFF-17-1.5	Suzhou Xiangcheng Zhengxu Wires and
T4 Cable	0.098" Dia, PTFE Jacket, 50 Ω , Semi-Flex Coax RG316U. 13" long, 4 turns	RG316 50 ohm	Belden
PCB	FR4 2.2mm 2 oz	D117914	MTL
Baseplate	A300X500T500D00	RFD190029	Machine Shop



Correlation data

Freq (MHz)	Span (MHz)	POUT (W)	GAIN (dB)	IRL (dB)	EFF (%)	IM3L (dBc)	IM3U (dBc)	ID1 (A)	VD1 (V)
1.8	0.01	200.9	24.6	-8.8	42.4	-34.7	-34.9	9.5	50.0
3.5	0.01	200.2	24.9	-12.5	45.0	-35.9	-35.8	8.9	50.0
7	0.01	200.4	24.9	-14.2	45.9	-40.4	-42.6	8.7	50.0
10	0.01	199.5	24.7	-14.7	45.4	-37.1	-39.3	8.8	50.0
20	0.01	200.0	23.6	-17.2	42.7	-30.2	-31.4	9.4	50.0
30	0.01	200.0	22.3	-19.3	40.1	-27.1	-28.1	10.0	50.0
50	0.01	199.5	20.4	-19.7	35.1	-25.8	-26.7	11.4	50.0
100	0.01	199.5	19.9	-26.5	38.5	-28.6	-29.1	10.4	50.0
150	0.01	200.4	18.7	-13.6	48.6	-28.6	-28.9	8.2	50.0

Average
power


IMD below 1 tone
Per MIL standart



Tuning tips


- Set I_{DQ} starts value to 500 mA by adjusting R2
- I_{DQ} affects efficiency and linearity (IM3). Usually higher I_{DQ} gives better linearity and lower efficiency.
- When adjusting R2, the I_{DQ} value should not be lower than 100 mA and higher than 1 A
- R7 – R12 are feedback resistors, they also affect efficiency and linearity. Higher resistor value gives better efficiency and lower linearity.

Test bench Setup

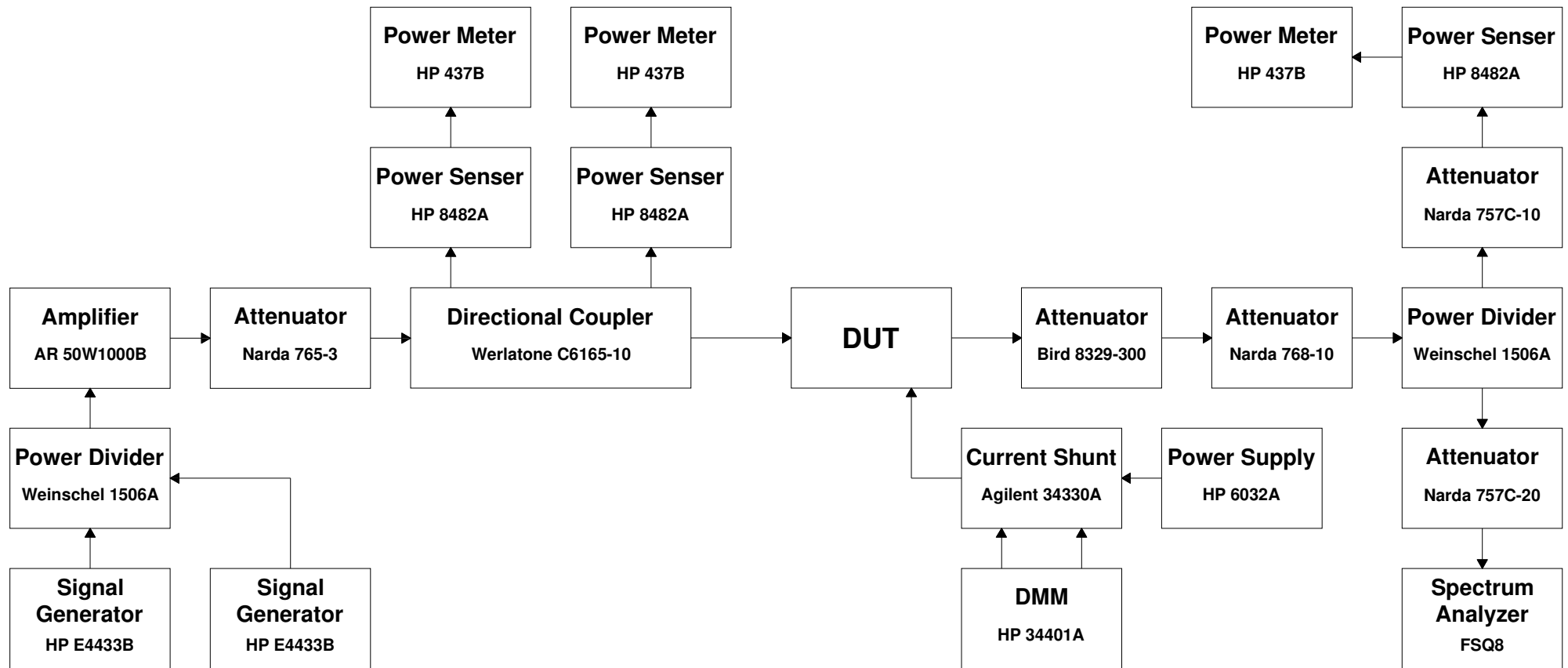


Frequency Sweep

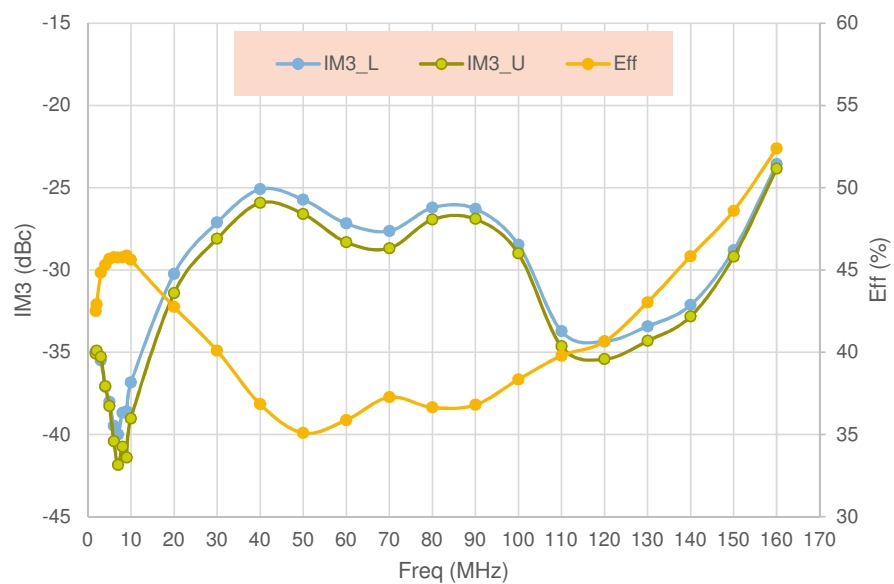MRF300NA/B push pull
2 tone, $P_{avg}=200W$



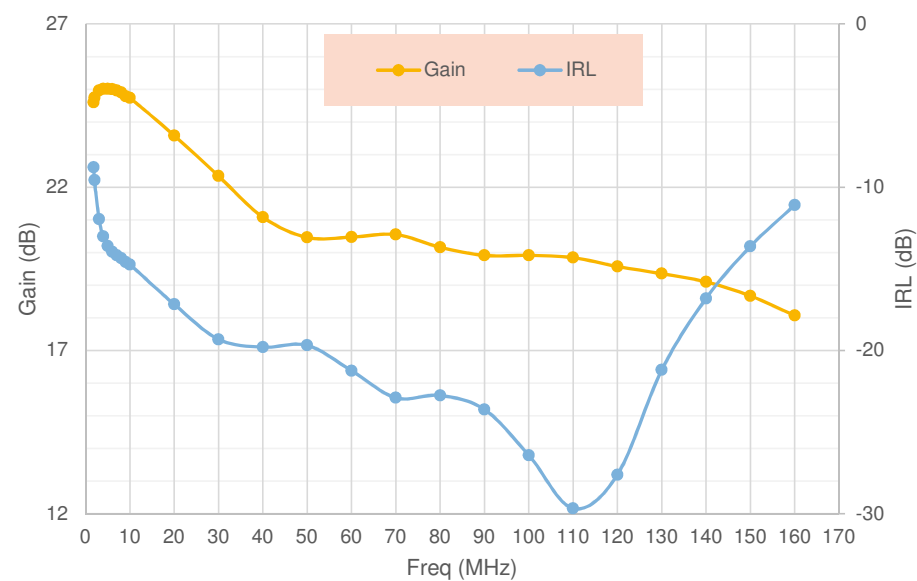MRF300NA/B push pull
2 tone, $P_{avg}=200W$





SECURE CONNECTIONS
FOR A SMARTER WORLD